

#### 4.9 Equivalent resistance

---

$$R_{eq} = \frac{R_5 \left[ \frac{R_1 R_2}{(R_1 + R_2)} + \frac{R_3 R_4}{(R_3 + R_4)} \right]}{R_5 + \frac{R_1 R_2}{(R_1 + R_2)} + \frac{R_3 R_4}{(R_3 + R_4)}}$$

#### 4.13 RLC circuit analysis

---

Component equations

$$i_{R_1} = \frac{e_0 - e_1}{R_1}$$

$$i_{R_2} = \frac{e_1}{R_2}$$

$$i_L = \frac{e_1 - e_2}{L D} \quad \text{with } i_L(0)$$

$$i_{C_2} = C_2 D e_2 \quad \text{with } e_2(0)$$

Node equations

$$i_{R_1} = i_{R_2} + i_L$$

$$i_L = i_{C_2}$$

Substitute component equations into node equations

$$\frac{e_0 - e_1}{R_1} = \frac{e_1}{R_2} + \frac{e_1 - e_2}{L D} \Rightarrow \left[ \frac{L D}{R_2} + \frac{L D}{R_1} + 1 \right] e_1 = \frac{L D}{R_1} e_0 + e_2$$

$$\frac{e_1 - e_2}{L D} = C_2 D e_2 \Rightarrow [L C_2 D^2 + 1] e_2 = e_1$$

Combine the above two equations

$$\left[ L D \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + 1 \right] \left[ L C_2 D^2 + 1 \right] e_2 - e_2 = \frac{L D}{R_1} e_0$$

Reduce

$$\left[ L C_2 D^2 + \frac{R_1 R_2 C_2}{(R_1 + R_2)} D + 1 \right] e_2 = \left( \frac{R_2}{R_1 + R_2} \right) e_0$$

The known initial conditions are  $i_L(0)$  and  $e_2(0)$ ; we need  $e_2(0)$  and  $\dot{e}_2(0)$ .

$$e_2(0) = \text{known}$$

$$\dot{e}_2(0) = \frac{1}{C_2} i_{C_2}(0) = \frac{1}{C_2} i_L(0) \quad (\text{from component equation and node equation})$$

$$\text{natural frequency} \quad \omega_n = \frac{1}{\sqrt{L C_2}}$$

$$\text{damping ratio} \quad \frac{2 \zeta}{\omega_n} = \frac{R_1 R_2 C_2}{(R_1 + R_2)} \quad \Rightarrow \quad \zeta = \frac{R_1 R_2}{2 (R_1 + R_2) \sqrt{\frac{L}{C_2}}}$$

$$\text{static gain} \quad G_s = \frac{R_2}{R_1 + R_2}$$

#### 4.16 RLC circuit transfer function \_\_\_\_

Component equations

$$i_{R_1} = \frac{e_0 - e_1}{R_1}$$

$$i_L = \frac{e_1 - e_2}{L D} \quad \text{with } i_L(0)$$

$$i_{C_1} = C_1 D e_2 \quad \text{with } e_2(0)$$

$$i_{R_2} = \frac{e_2 - e_3}{R_2}$$

$$i_{C_2} = C_2 D e_3 \quad \text{with } e_3(0)$$

Node equations

$$i_{R_1} = i_L, \quad i_L = i_{C_1} + i_{R_2}, \quad i_{R_2} = i_{C_2}$$

Substitute component equations into node equations.

$$\frac{e_0 - e_1}{R_1} = \frac{e_1 - e_2}{L D} \quad \text{or} \quad \left[ \frac{L}{R_1} D + 1 \right] e_1 = \frac{L D}{R_1} e_0 + e_2$$

$$\frac{e_1 - e_2}{L D} = C_1 D e_2 + \frac{e_2 - e_3}{R_2} \quad \text{or} \quad \left[ L C_1 D^2 + \frac{L}{R_2} D + 1 \right] e_2 = \frac{L D}{R_2} e_3 + e_1$$

$$\frac{e_2 - e_3}{R_2} = C_2 D e_3 \quad \text{or} \quad [R_2 C_2 D + 1] e_3 = e_2$$

Reduce to get  $e_3$  as a function of  $e_0$ .

$$\frac{e_3}{e_0} = \frac{1}{R_2 C_2 L C_1 D^3 + (L C_1 + L C_2 + R_1 C_1 R_2 C_2) D^2 + (R_1 C_1 + R_2 C_2 + R_1 C_2) D + 1}$$

#### 4.17 RLC circuit state-space derivation \_\_\_\_\_

Component equations

$$i_{R_1} = \frac{e_0 - e_1}{R_1}$$

$$i_L = \frac{e_1 - e_2}{L D} \quad \text{with } i_L(0)$$

$$i_{C_1} = C_1 D e_2 \quad \text{with } e_2(0)$$

$$i_{R_2} = \frac{e_2 - e_3}{R_2}$$

$$i_{C_2} = C_2 D e_3 \quad \text{with } e_3(0)$$

Node equations

$$i_{R_1} = i_L, \quad i_L = i_{C_1} + i_{R_2}, \quad i_{R_2} = i_{C_2}$$

From the component equations, we can select state variables as follows.

$$u_1 = e_0$$

$$x_1 = i_L \quad \text{thus} \quad \dot{x}_1 = D i_L = \frac{e_1 - e_2}{L} = \frac{1}{L} e_1 - \frac{1}{L} x_2$$

$$x_2 = e_2 \quad \text{thus} \quad \dot{x}_2 = D e_2 = \frac{1}{C_1} i_{C_1}$$

$$x_3 = e_3 \quad \text{thus} \quad \dot{x}_3 = D e_3 = \frac{1}{C_2} i_{C_2}$$

We need to eliminate  $e_1$ ,  $i_{C_1}$ , and  $i_{C_2}$ . From the  $R_1$  component equation and the first node equation,

$$e_1 = e_0 - R_1 i_{R_1} = e_0 - R_1 i_L = u_1 - R_1 x_1$$

From the second node equation and the  $R_2$  component equation,

$$i_{C_1} = i_L - i_{R_2} = i_L - \frac{e_2 - e_3}{R_2} = x_1 - \frac{1}{R_2} x_2 + \frac{1}{R_2} x_3$$

From the last node equation and the  $R_2$  component equation,

$$i_{C_2} = i_{R_2} = \frac{e_2 - e_3}{R_2} = \frac{1}{R_2} x_2 - \frac{1}{R_2} x_3$$

State-space representation

$$\dot{x}_1 = -\frac{R_1}{L} x_1 - \frac{1}{L} x_2 + \frac{1}{L} u_1$$

$$\dot{x}_2 = \frac{1}{C} x_1 - \frac{1}{R_2 C_1} x_2 + \frac{1}{R_2 C_1} x_3$$

$$\dot{x}_3 = \frac{1}{R_2 C_2} x_2 - \frac{1}{R_2 C_2} x_3$$

With the initial conditions

$$x_1(0) = i_L(0)$$

$$x_2(0) = e_2(0)$$

$$x_3(0) = e_3(0)$$

#### 4.25 Dual op-amp filter circuit

---

The two op-amp circuits can be treated independently since the output of each acts like a voltage source to the next stage. For the first op-amp, the two resistances  $R$  are the same thus, the circuit is an inverter.

$$e_1 = -e_i$$

The second op-amp circuit is a low-pass filter.

$$e_2 = \frac{-\frac{R_f}{R_i}}{R_f C_f D + 1} e_1$$

The second op-amp drives the  $RC$  circuit.

$$e_o = \frac{1}{R_L C_L D + 1} e_2$$

Combining,

$$e_o = \left[ \frac{1}{R_L C_L D + 1} \right] \left[ \frac{\frac{R_f}{R_i}}{R_f C_f D + 1} \right] e_i = \frac{\frac{R_f}{R_i} e_i}{R_L C_L R_f C_f D^2 + (R_L C_L + R_f C_f) D + 1}$$

The static gain is  $G_s = \frac{R_f}{R_i}$

Using  $\tau_L = R_L C_L$  and  $\tau_f = R_f C_f$

The natural frequency is  $\omega_n = \sqrt{\frac{1}{R_L C_L R_f C_f}} = \sqrt{\frac{1}{\tau_L \tau_f}}$

The damping ratio is  $\zeta = \frac{(R_L C_L + R_f C_f)}{2\sqrt{R_L C_L R_f C_f}} = \frac{(\tau_L + \tau_f)}{2\sqrt{\tau_L \tau_f}}$

Using the values stated,  $\frac{R_f}{R_i} = 1$

$$\tau_L = 500 \text{ ohm } 10 \times 10^{-6} \frac{\text{s}}{\text{ohm}} = 0.005 \text{ s}$$

$$\tau_f = 10 \times 10^3 \text{ ohm } 1 \times 10^{-6} \frac{\text{s}}{\text{ohm}} = 0.010 \text{ s}$$

Thus, the static gain is  $G_s = 1$

The natural frequency is  $\omega_n = \sqrt{\frac{1}{0.005 \text{ s} \times 0.010 \text{ s}}} = 27.1 \frac{\text{rad}}{\text{s}} = 4.32 \text{ Hz}$

The damping ratio is  $\zeta = \frac{(0.005 + 0.010)}{2\sqrt{0.005 \times 0.010}} = 0.204$

#### 4.26 Dual op-amp filter state-space derivation \_\_\_\_\_

From the analysis in Problem 4.25, the modeling equations are

$$e_2 = \frac{G_s}{\tau_f D + 1} e_i \quad \text{with } e_2(0)$$

$$e_o = \frac{1}{\tau_L D + 1} e_2 \quad \text{with } e_o(0)$$

where  $G_s = \frac{R_f}{R_i}$      $\tau_L = R_L C_L$     and     $\tau_f = R_f C_f$

The state-space representation for this system is

$$u_1 = e_i$$

$$x_1 = e_2 \quad \text{thus} \quad \dot{x}_1 = D e_2 = \frac{-x_1 + G_s u_1}{\tau_f}$$

$$x_2 = e_o \quad \text{thus} \quad \dot{x}_2 = D e_o = \frac{-x_2 + x_1}{\tau_L}$$

### 4.30 Voltmeter measurement degradation

---

The transfer function of the original circuit is

$$e_1 = \frac{1}{1 + \frac{10,000}{47,000}} e_0 = 0.8246 e_0$$

The transfer function of the circuit with the voltmeter is

$$e_1 = \frac{1}{1 + \frac{10,000}{47,000} \left( 1 + \frac{47,000}{R_{meter}} \right)} e_0$$

If  $R_{meter} = 100 \text{ k}\Omega$ , then voltage reading will be degraded by 7.6 % (i.e., volt reading = 92.4 % of undisturbed voltage).

If  $R_{meter} = 1 \text{ M}\Omega$ , then voltage reading will be degraded by 0.8 %.

Case Simulation Study: